

# **CPU Architecture**

**LAB2 preparation report**

**VHDL part2**

**Sequential code and Behavioral modeling**

**Hanan Ribo**

**16/04/2020**

## Table of contents

1.	Aim of the Laboratory .....	3
2.	System Design definition.....	3
3.	Test and Timing:.....	4
4.	Requirements .....	4
5.	Grading Policy .....	5

# 1. Aim of the Laboratory

- Obtaining skills in VHDL part2 code, which contains Sequential code and Behavioral modeling.
- Obtaining basic skills in ModelSim (multi-language HDL simulation environment).
- knowledge in digital systems design.
- Proper analysis and understanding of architecture design.

## 2. System Design definition

In this laboratory you will design a synchronous digital system which detects valid sub series for a given condition value (see table 1). The system block diagram is depicted in figure 1, you are required to design the whole system and make a test bench for testing.

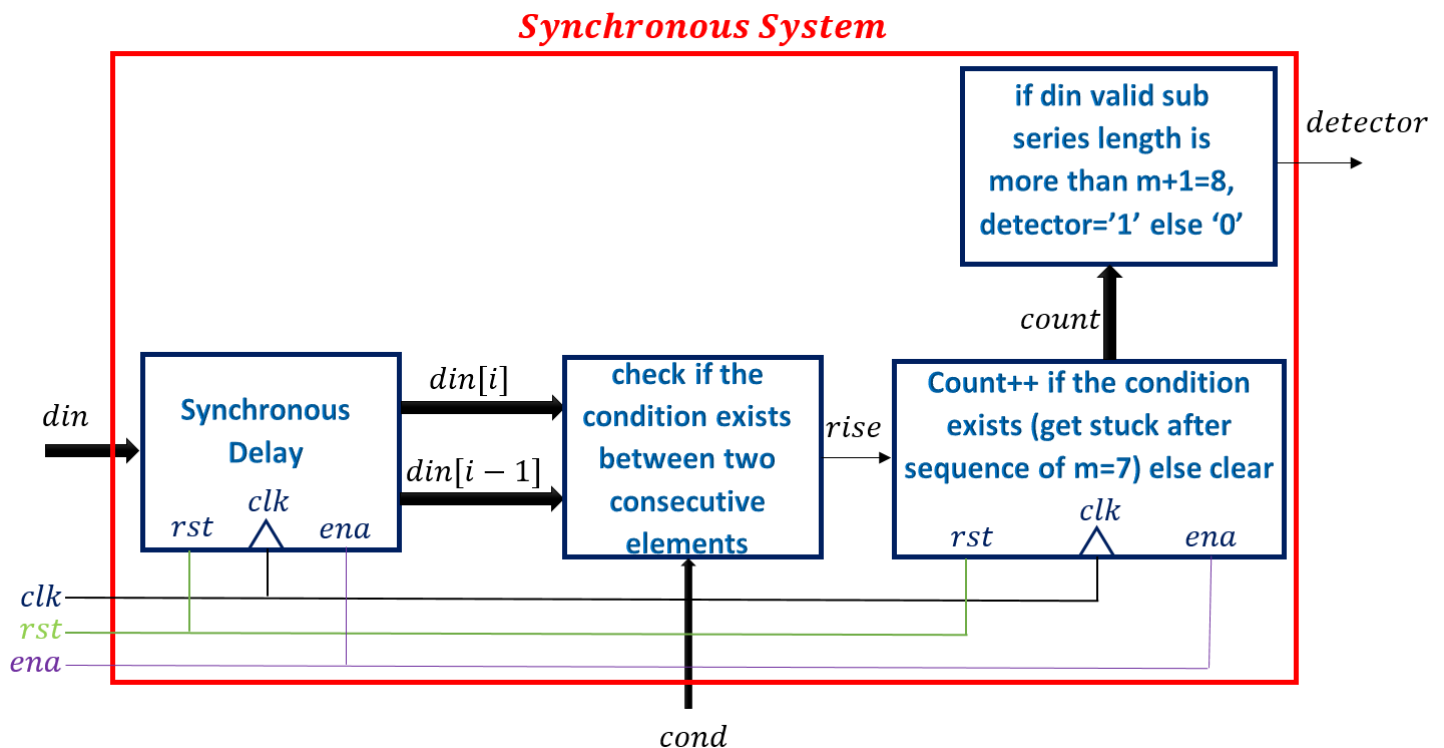


Figure 1 : System structure

cond	Condition type	Explanation
0	$din[i] - din[i - 1] = 1$	ascending sub series by 1
1	$din[i] - din[i - 1] = 2$	ascending sub series by 2
2	$din[i] - din[i - 1] = 3$	ascending sub series by 3
3	$din[i] - din[i - 1] = 4$	ascending sub series by 4

Table 1: cond value

- The Top Level design modeling can be Behavioral except the **Adder** based condition check module (single instantiation only of **Adder.vhd**). The main reason of this constraint is to minimize HW.
- you are given the next three files that you must use in your project: **top.vhd**, **aux\_package.vhd**, **Adder.vhd** (you can only add your code to **top.vhd** file, you are not allowed to erase nothing).
- Examples:

 


Figure 2: examples using waveforms

### 3. Test and Timing:

- Design a test bench which tests all the system.
- Analyze the results by zooming on the important transactions in the waveforms. explain these (input/output/internal signals of the system).
- You are welcome to use the Internet also as reference.
- The timing of the system will be ideal (means a functional simulation).


### 4. Requirements

- The design must be well commented.
- Important:** For each of two submodules:
  - Graphical description (a square with ports going in and out) and short descriptions.
- Elaborated analysis and wave forms:
  - Remove irrelevant signals.
  - Zoom on regions of interest.
  - Draw clouds on the waveform with explanations of what is happening (Figure 4).
  - Change the waveform colors in ModelSim for clear documentation  
(Tools->Edit Preferences->Wave Windows).

- d. A ZIP file in the form of **id1\_id2.zip** (where id1 and id2 are the identification number of the submitters, and  $id1 < id2$ ) must be upload to Moodle only by id1 student. The ZIP file will contain:

Directory	Contains	Comments
VHDL	Project VHDL files	Only VHDL files, excluding test bench <b>Note: your project files must be well compiled without errors as a basic condition before submission</b>
TB	VHDL files that are used for test bench	
SIM	DO files of wave and list forms	Only for <b>tb.vhd</b>
DOC	Project documentation	<b>Readme.txt</b> and <b>pre2.pdf</b> report file

**Table 2: Directory Structure**

 

**Figure 3: Clouds over the waveform example**

## 5. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done
90%	Analysis and Test	The correct analysis of the system (under the requirements)

**Table 1 : Grading**

Under the above policies you'll be also evaluated using common sense:

- Your files will be compiled and checked, the system must work.
- Your design and architecture must be intelligent, minimal, effective and well organized.

**For a late submission the penalty is 2<sup>day</sup>**

